

EE 282


HW #5

Due: May 6, 2011

- ① For the basic TTL inverter shown below, determine I_{IN} , I_{RB} , I_{B0} , I_{RC} for the following conditions.

a) $V_{IN} = 0V$

b) $V_{IN} = 5V$

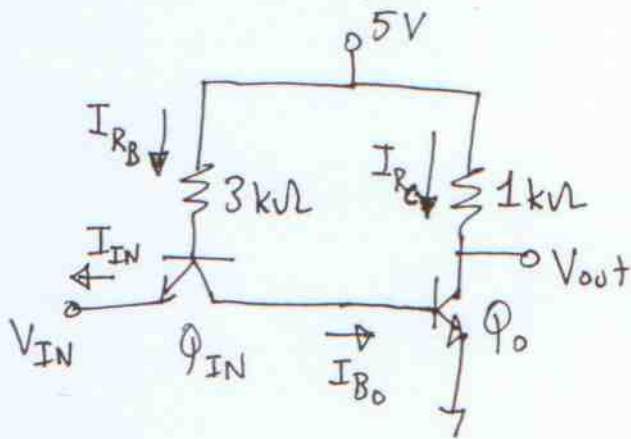

$$\beta_F = 100$$

$$V_{BE}(FA) = V_{BE}(RA) = 0.7V$$

$$V_{BE}(SAT) = 0.8V$$

$$V_{CE}(SAT) = 0.2V$$

$$\beta_R = 0.1$$

- ② Sketch VTC of the gate in problem 1.

- ③ Calculate the fan-out of the gate in problem 1; if V_{OH} of the driver gate is allowed to 1V voltage drop from no-load condition and driver is allowed to absorb current such that Q_O is saturated at most with the saturation parameter of 0.85.