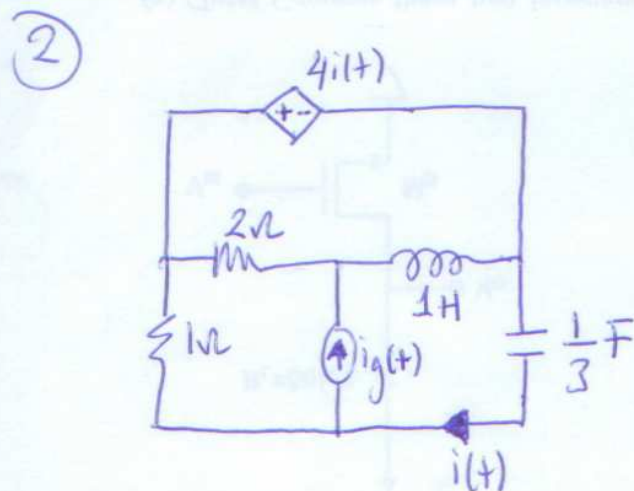


a) Apply a source-shift transformation so that circuit can be partitioned into generalized branches.


b) Write node equations using graph theoretical methods. (Show matrices; but do NOT multiply matrices at the last stage; just show which matrices should be multiplied).
Find initial conditions for node voltages.

c) Find a tree such that whose fun. cut-set equations are exactly the same equations you have found in part b. How many such trees are there?




Find state equations.

a)

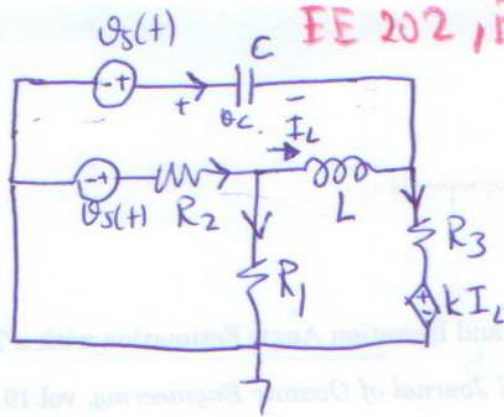

b)

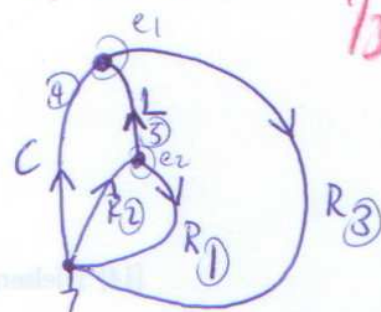

$$\textcircled{1} \quad \underline{A} \underline{J} = \underline{0} \longrightarrow \begin{bmatrix} 0 & 0 & 1 & -1 & -1 \\ 1 & -1 & 0 & 0 & 1 \end{bmatrix} \begin{bmatrix} J_1 \\ J_2 \\ J_3 \\ J_4 \\ J_5 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \end{bmatrix}$$

$$\textcircled{2} \quad \underline{A}^T \underline{e} = \underline{v}$$

$$\begin{bmatrix} 0 & 1 \\ 0 & -1 \\ 1 & 0 \\ -1 & 0 \\ -1 & 1 \end{bmatrix} \begin{bmatrix} e_1 \\ e_2 \end{bmatrix} = \begin{bmatrix} \vartheta_1 \\ \vartheta_2 \\ \vartheta_3 \\ \vartheta_4 \\ \vartheta_5 \end{bmatrix}$$

$$\textcircled{3} \quad J_1 = \frac{\vartheta_1}{R_1}; \quad J_2 = \frac{\vartheta_2 + \vartheta_5}{R_2}; \quad J_3 = \frac{\vartheta_3 - k I_L(t)}{R_3} = \frac{\vartheta_3 - k (I_L(t) + \frac{1}{L} \int_0^t \vartheta_5(z) dz)}{R_3}$$


$$J_5 = I_L(t) + \frac{1}{L} \int_0^t \vartheta_5(z) dz; \quad J_4 = C \frac{d}{dt} [\vartheta_4(t) + \vartheta_5(t)]$$

$$\begin{bmatrix} J_1 \\ J_2 \\ J_3 \\ J_4 \\ J_5 \end{bmatrix} = \begin{bmatrix} 1/R_1 & 0 & 0 & 0 & 0 \\ 0 & 1/R_2 & 0 & 0 & 0 \\ 0 & 0 & 1/R_3 & 0 & -k/LR_3 \\ 0 & 0 & 0 & C & 0 \\ 0 & 0 & 0 & 0 & 1/L \end{bmatrix} \begin{bmatrix} \vartheta_1 \\ \vartheta_2 \\ \vartheta_3 \\ \vartheta_4 \\ \vartheta_5 \end{bmatrix} + \begin{bmatrix} 0 \\ \vartheta_5/R_2 \\ -kI_0/R_3 \\ C D \vartheta_5(t) \\ I_0 \end{bmatrix}$$

$$\underline{J} = \underline{G}(s) \underline{v} + \underline{\text{Source}}$$

At $t=0^+$

2/3

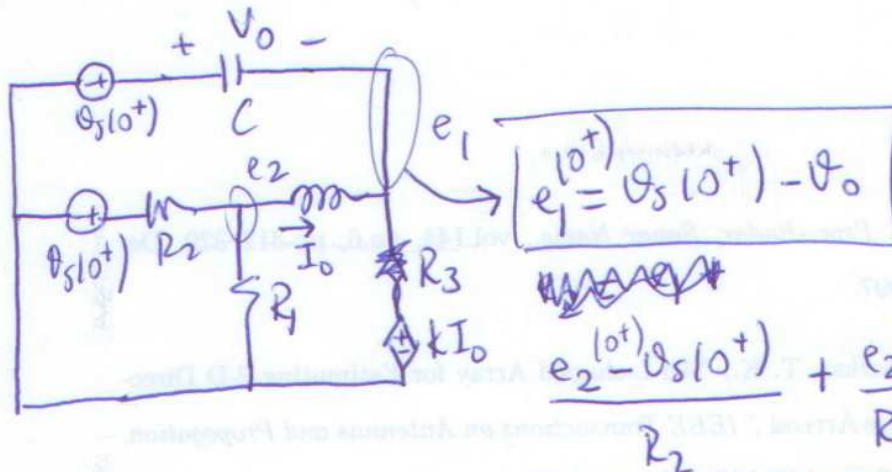

$$\frac{e_2^{(0+)} - \vartheta_s(0^+)}{R_2} + \frac{e_2^{(0+)}}{R_1} + I_0 = 0.$$

$$e_2^{(0+)} = \left(\frac{1}{R_2} + \frac{1}{R_1} \right)^{-1} \left[\frac{\vartheta_s(0^+)}{R_2} - I_0 \right]$$

c) F-Cut-sets include only one branch from tree.

then Fun Cut Set 1 has $\{C, L, R_3\}$ branches.

Fun Cut Set 2 has $\{R_1, R_2, L\}$ branches.

then x can not be a tree branch. (appears in two different fun. cut set), but all other combinations are feasible. $\{C, R_1\}, \{C, R_2\}, \{R_3, R_1\}, \{R_3, R_2\}$.



1) cont

$$\underline{A_s} \underline{e} = 0 \rightarrow \underline{A_s} = \overbrace{A(G(D) \frac{\vartheta}{1} + \underline{\text{source}})}^3 = 0.$$

$$= \overbrace{A(G(D) A^T \underline{e} + \underline{\text{source}})}^3 = 0.$$

$$\left(\underset{2 \times 2}{A} \underset{2 \times 2}{G(D)} \underset{2 \times 2}{A^T} \right) \underset{2 \times 1}{\underline{e}} = \underbrace{-A \text{ source}}_{2 \times 1} \overset{[e_1 \ e_2]^T}{\leftarrow}$$

(2)

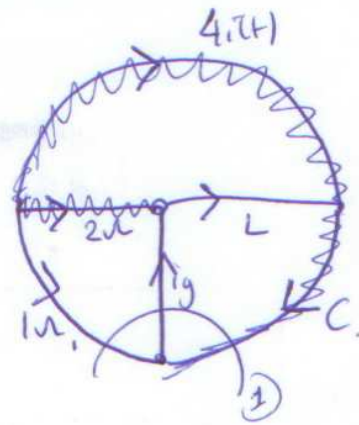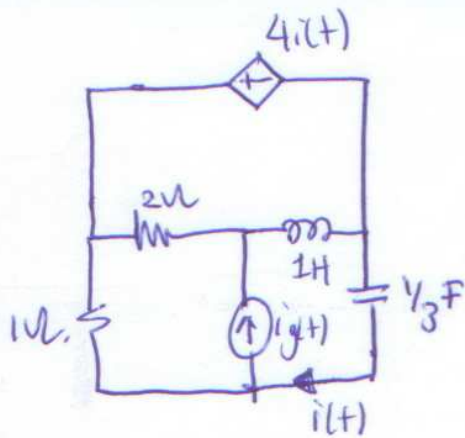

State Var. = $\{i_L, v_C\}$.

$$\begin{aligned} \textcircled{1} \quad C \dot{v}_C &= i_g(t) - i_{1\Omega} = i_g(t) - \frac{v_{1\Omega}}{1} = i_g(t) - \frac{4i_L(t) + v_C}{1} \\ &= i_g(t) - 4C \dot{v}_C - v_C. \end{aligned}$$

$$\boxed{\dot{v}_C = -\frac{3}{5} v_C + \frac{3}{5} i_g(t)}$$

$$\begin{aligned} \textcircled{2} \quad L \dot{i}_L(t) &= -v_{2\Omega} + 4i(t) \\ &= -i_{2\Omega} \cdot 2 + 4 \frac{1}{3} \dot{v}_C \\ &= -(i_L - i_g) 2 + \frac{4}{5} v_C + \frac{4}{5} i_g(t). \end{aligned}$$

$$\boxed{\dot{i}_L(t) = -\frac{4}{5} v_C - 2i_L + \frac{14}{5} i_g(t)}$$