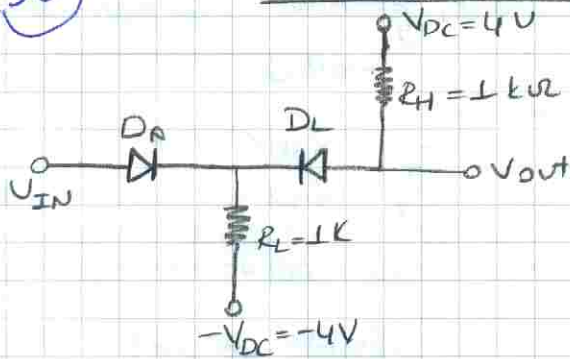


EE-282 HOMEWORK - III

30


1)



Because $-V_{DC} < V_{IN} < V_{DC}$
 $-4V < V_{IN} < 4V$

Graph is bounded by $V_{IN} = -4V$ & $V_{IN} = 4V$

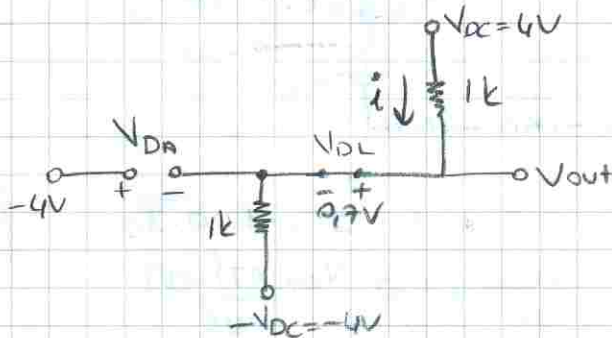Assume that D_A is OFF and D_L is ON when $V_{IN} = -4V$



$$i = \frac{4 - (-4) - 0.7}{2k} = \frac{7.3}{2k} = 3.65 \text{ mA}$$

$i = 3.65 \text{ mA} > 0$ (So assumption which is D_L is ON, is TRUE)

$$V_{DA} = -4 - (4 - 3.65 - 0.7) \\ = -4 - (-0.35) \\ = -4 + 0.35 = -3.65 < 0$$


(So assumption which is D_A is OFF, is TRUE)

$$\text{Then } V_{out} = 4 - 3.65 = 0.35 \text{ V}$$

When V_{IN} reaches 0.35 V , D_A becomes ON. Because,


$$V_{DA} = 0.35 - (-0.35) = 0.7 \text{ V}$$

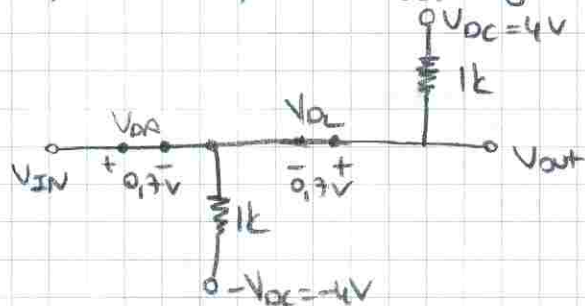After that point V_{out} begins to increase




As V_{IN} increases, V_{out} increases at the same rate. Because V_{DA} and V_{DL} cancels each other, and $V_{IN} = V_{out}$


So the graph should be

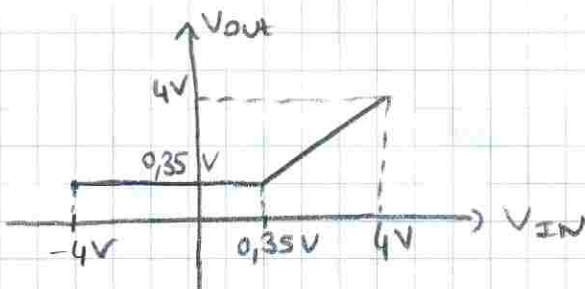

2) (30)

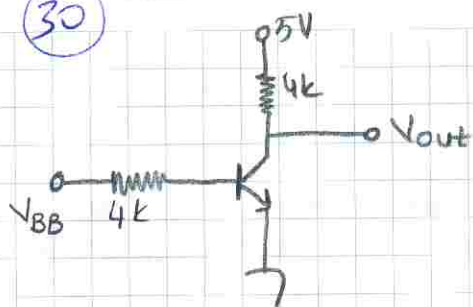

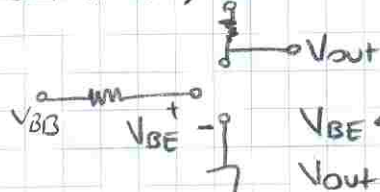
When $0 < V_{BB} < 0.7V$, the transistor is in OFF mode, because $V_{BE} < 0.7V$




$V_{BE} < 0.7V$
 $V_{out} = 5V$, since there is no current.

When $V_{BB} = 0.7$, the transistor turns on and passes to the Forward Active mode.

In FA;

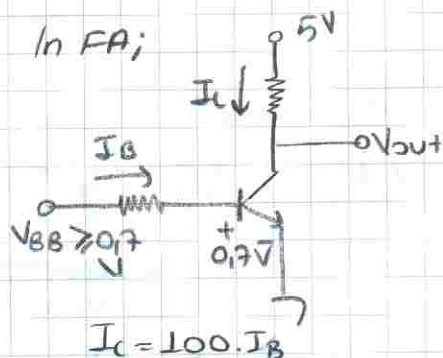

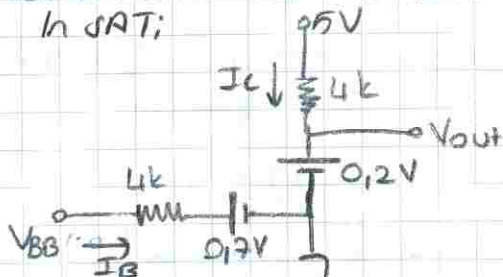Then transistor reaches saturation model
In SAT;



At SAT point, $I_C = 100 \cdot I_B$


$$\frac{5 - 0.2}{4k} = 100 \cdot \frac{V_{BB(SAT)} - 0.7}{4k}$$

$$0.1048 = V_{BB(SAT)} - 0.7$$

$$V_{BB(SAT)} = 0.748V$$

$$\text{and } V_{out} = 0.2V$$


So the VTC;

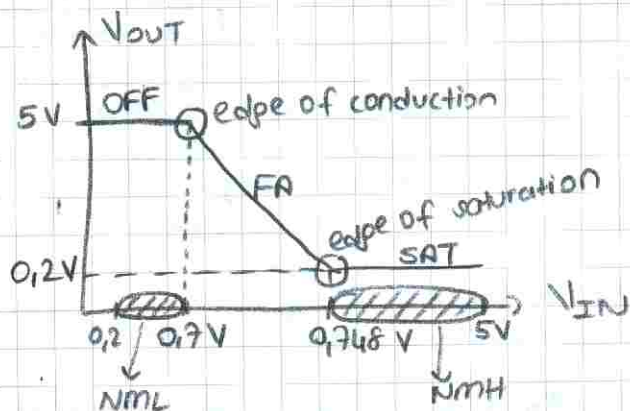


$$NMH = V_{OH} - V_{IH} = 5V - 0.748V = 4.252V$$

$$NML = V_{OL} - V_{IL} = 0.7V - 0.2V = 0.5V$$


3) 40

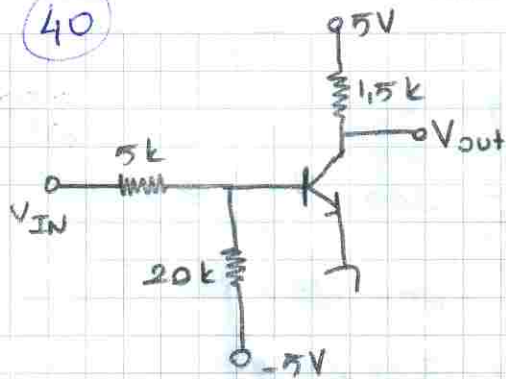


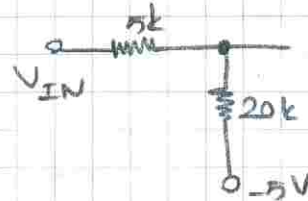
In order to solve the problem, first we should find the Thevenin equivalent of the left hand side.



$$R_{TH} = 5k \parallel 20k = 4k$$

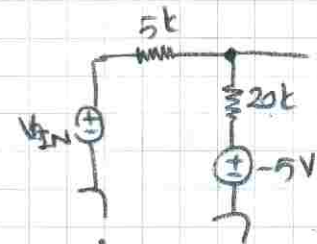

To find R_{TH}
kill the sources

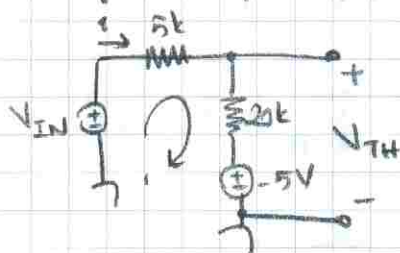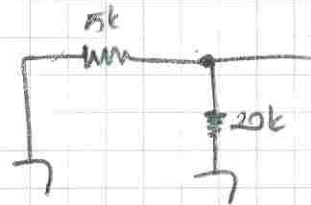


KVL

$$-V_{IN} + 5k i + 20k i - 5 = 0$$


$$i = \frac{V_{IN} + 5}{25k}$$

$$V_{TH} = 20k \cdot \frac{V_{IN} + 5}{25k} - 5 = \frac{4V_{IN} + 20 - 25}{5} = \frac{4V_{IN} - 5}{5}$$

So the circuit changes to,

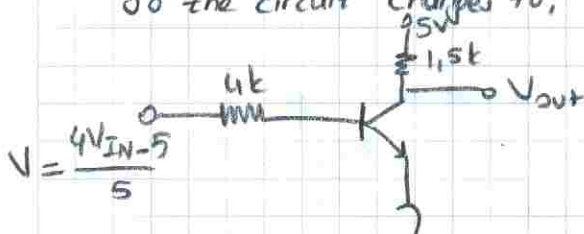


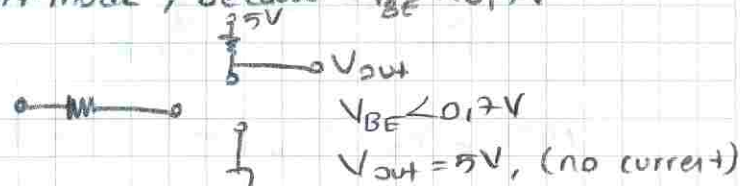When $0 < V < 0.7V$, the transistor is in OFF mode, because $V_{BE} < 0.7V$



When $V = 0.7V$, the transistor turns on and passes to Forward Active mode.
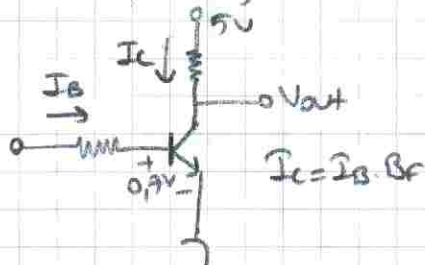
$$V = 0.7V = \frac{4V_{IN} - 5}{5} \Rightarrow V_{IN} = \frac{8.5}{4} = 2.125V \text{ (When transistor is at the edge of conduction)}$$



Then transistor reaches SAT mode!

\Rightarrow