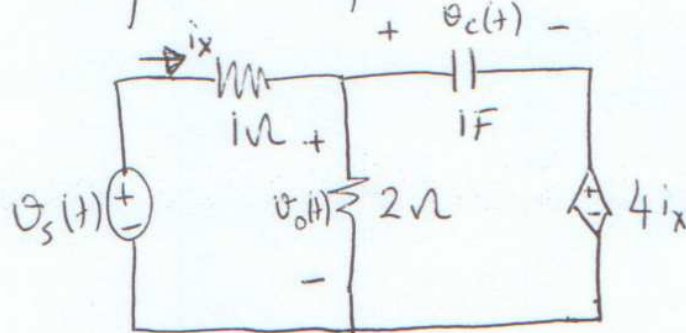


a) Find Thevenin equivalent of the circuit seen from a-b terminals for the steady-state operation with  $i_s(t) = \cos(2t)$ .

b) Using part a, find  $i_L^{ss}(t)$

c) Find  $i_L^{ss}(t)$  when  $i_s(t) = 1A$ .

② a) Using Thevenin-Norton equivalent find  $V_o(t)$  with Laplace Transform (Laplace Domain) methods.




$$V_s(t) = 5u(t) ; V_c(0^-) = 0V$$

b) Find zero input solution of the circuit given in part a) if  $V_c(0^-) = V_0$  Volts, for the circuit variable  $V_o(t)$ .


— Exam 3 —

— Solutions —

① a)  $V_{oc} = ?$

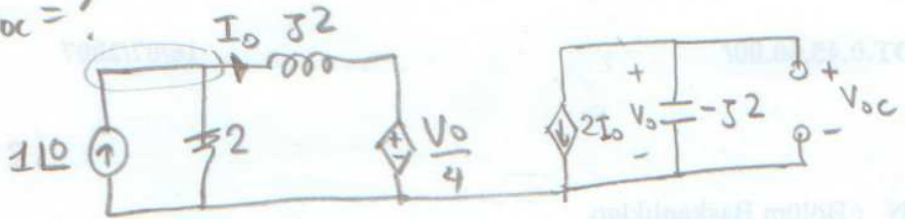
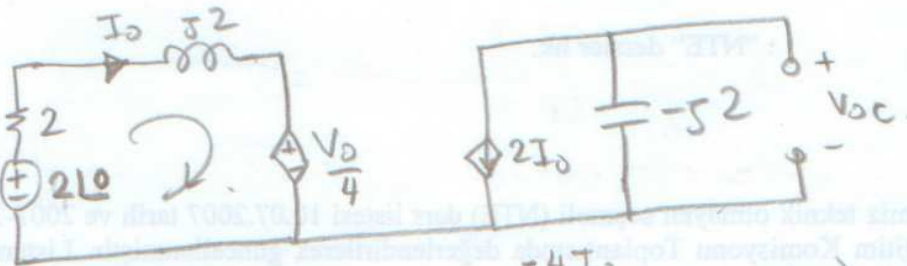
$$V_o = V_{oc} = (-j2)(-2I_o) = j4I_o \quad (1)$$




$$-2 + 2I_o + j2I_o + \frac{V_o}{4} = 0 \quad (2)$$

$$I_o = \frac{2}{2+j3} = \frac{2}{13}(2-j3)$$

$$V_{oc} = \frac{8}{13}(3+j2) \quad \text{from (1)}$$

$i_{sc} = ?$

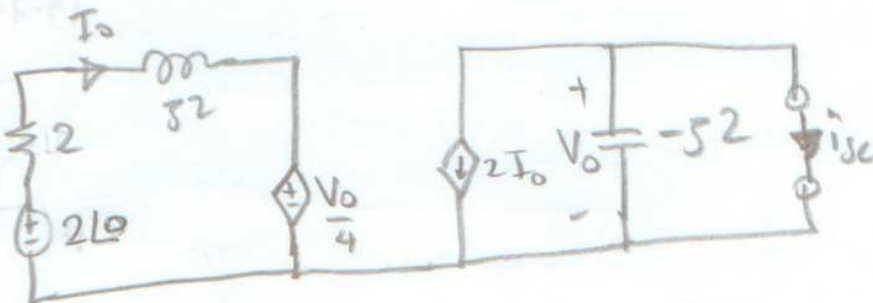



$$i_{sc} = -2I_o ; \rightarrow V_o = 0 \rightarrow \text{from (2)} \rightarrow I_o = \frac{2}{2+j2}$$

$$i_{sc} = \frac{-2}{1+j} = -(1-j)$$

$$Z_{in} = \frac{V_{oc}}{I_{sc}} = \frac{\frac{8}{13}(3+2j)}{-(1-j)} = -\frac{4}{13}(3+2j)(1+j)$$

$$= -\frac{4}{13}(1+5j)$$

(2)

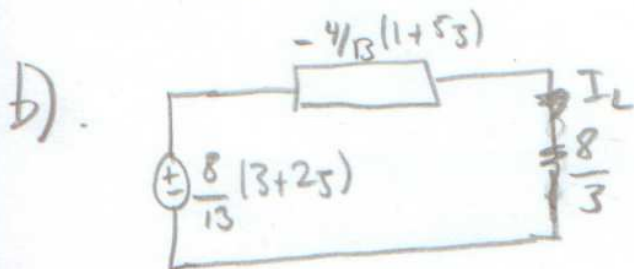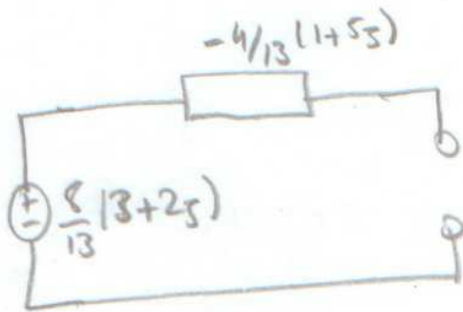


$$I_L = \frac{\frac{8}{13}(3+2j)}{-\frac{4}{13}(1+5j) + \frac{8}{3}} = \frac{24(3+2j)}{-12+10j-60j}$$

$$I_L = \frac{24}{4} \frac{(3+2j)}{(23-15j)}$$

$$= \frac{6}{23^2+15^2} (39+j91)$$

$$= 0.31 + j0.72 = 0.78 \angle 66.2^\circ$$
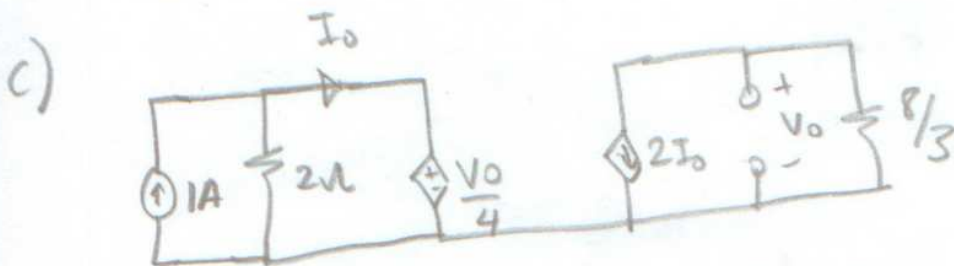
$$I_L(t) = 0.78 \cos(2t + 66.2^\circ) \text{ A.}$$




$$V_0 = -\frac{8}{3} \cdot 2I_0 ; I_0 = \frac{-V_0}{8} + 1$$

$$I_0 = \frac{2}{3} I_0 + 1 \rightarrow I_0 = +3 \text{ A.}$$

$$\downarrow$$

$$V_0 = -16 \text{ V}$$

$$i_2^{ss}(t) = 3 \text{ A.}$$

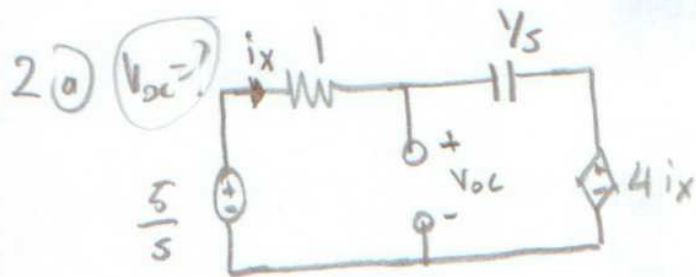


$$i_x = \frac{5/s}{1 + 1/s + 4} = \frac{5}{5s+1}$$

3

$$V_{oc} = 4i_x + \frac{1}{s}i_x = \left(\frac{4s+1}{s}\right)i_x$$
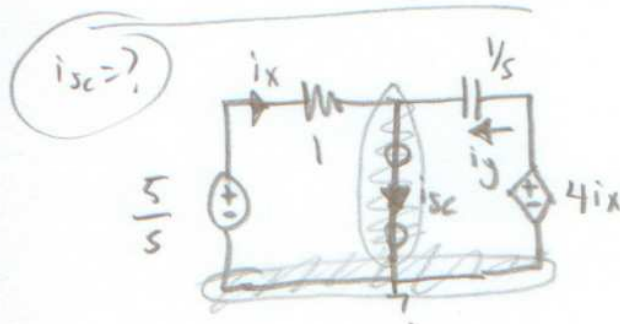
$$V_{oc} = \frac{5}{s} \frac{4s+1}{5s+1}$$




$$i_x = 5/s$$

$$i_y = \frac{4i_x}{1/s} = 20$$

$$\left. \begin{aligned} i_x &= 5/s \\ i_y &= 20 \end{aligned} \right\} \begin{aligned} i_{sc} &= i_x + i_y \\ &= \frac{5}{s} + 20 \end{aligned}$$

$$i_{sc} = \frac{5(1+4s)}{s}$$
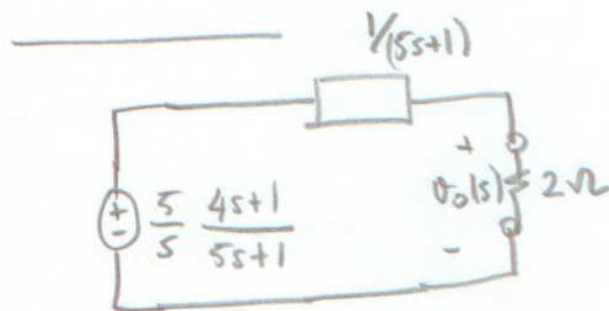
$$R_{Th}(s) = \frac{\frac{5}{s} \frac{(1+4s)}{(5s+1)}}{\frac{5}{s} (1+4s)} = \frac{1}{5s+1}$$



$$V_0(s) = \frac{5}{s} \frac{4s+1}{5s+1} \cdot \frac{2}{2 + \frac{1}{5s+1}} =$$


$$= \frac{5}{s} \frac{4s+1}{5s+1} \cdot \frac{2}{\frac{10s+3}{5s+1}} = \frac{10}{s} \frac{4s+1}{10s+3} = \frac{4(s+1/4)}{s(s+0.3)}$$

$$V_0(s) = \frac{A}{s} + \frac{B}{s+0.3} = \frac{1/0.3}{s} + \frac{\frac{4}{+0.3} \cdot 0.05}{s+0.3} = \frac{3.\bar{3}}{s} + \frac{0.\bar{6}}{s+0.3}$$



$$v_o(t) = \left( 3.3 + 0.6 e^{-0.3t} \right) v(t)$$

(4)

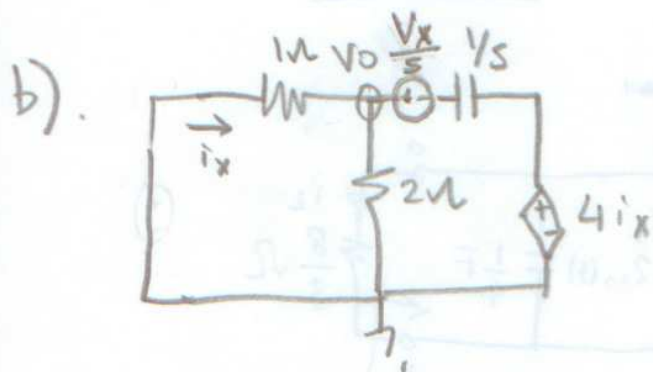

$$v_c(0^-) = V_x$$


$$\frac{V_o(s)}{2} + \frac{V_o(s)}{1} + \frac{V_o(s) - V_x/s - 4ix}{1/s} = 0$$

$$V_o(s) \left[ \frac{3}{2} + s \right] = V_x$$

$$V_o(s) = \frac{V_x}{\frac{3}{2} + s} = \frac{V_x/s}{s + 0.3}$$

$$V_o(t) = \frac{V_x}{s} e^{-0.3t} - v(t)$$

$$v_c(0^-)$$

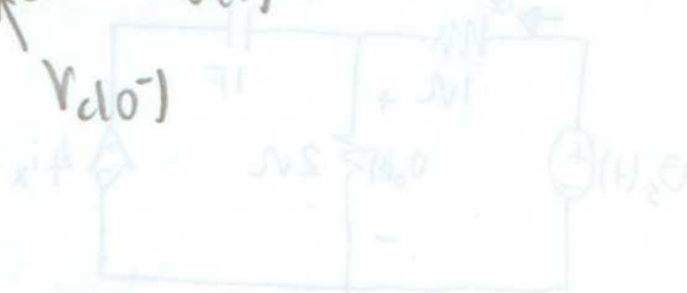

$$v_o(t) = 3.3 + 0.6 e^{-0.3t}$$