

**EE 202**  
**Homework #1**  
(Due: March 2, 2006)

- 1) The natural response of a 2<sup>nd</sup> order circuit for two sets of initial conditions at time  $t = 0$  is given as follows :


Set 1	Set 2
$V_c(t) = 2e^{-2t} u(t)$	$V_c(t) = 4e^{-3t} u(t)$
$i_L(t) = 1e^{-2t} u(t)$	$i_L(t) = 8e^{-3t} u(t)$

a) Find the form of the solution for  $\begin{bmatrix} V_c(t) \\ i_L(t) \end{bmatrix}$

b) Tell how the order of the circuit relates to number of dynamic components. What are the natural frequencies of the circuit?

c) Find a circuit such that it has all passive elements and independent sources and its natural frequencies are on the imaginary axis.


2)

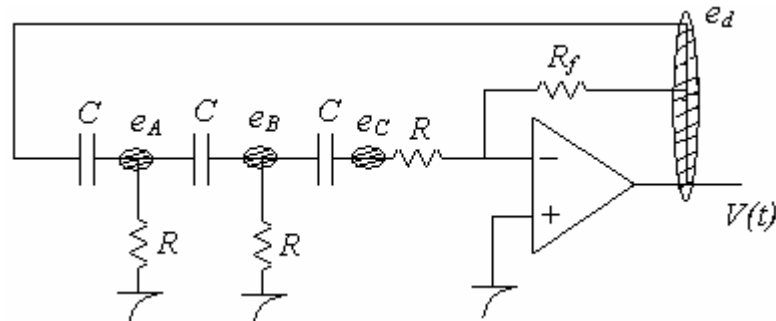


Op-Amp is assumed to be in linear region.

- First express  $e_d$  in terms of  $e_A$ ,  $e_B$  and  $e_C$  then write node equations in terms of  $e_A$ ,  $e_B$ ,  $e_C$ . (You should have a 3x3 matrix differential equation.)
- For  $R = 1\Omega$  ;  $C = 1F$  , find  $R_f$  so that circuit has a natural frequency at  $s = -\frac{1}{6}$ .  
What are the other natural frequencies? Is this circuit stable?

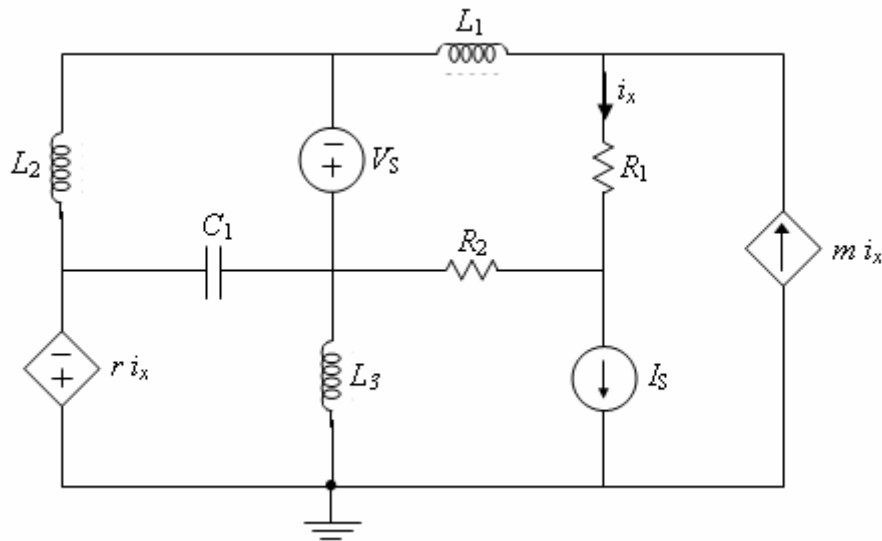
3) Write **Node, Mesh equations** for the circuit.



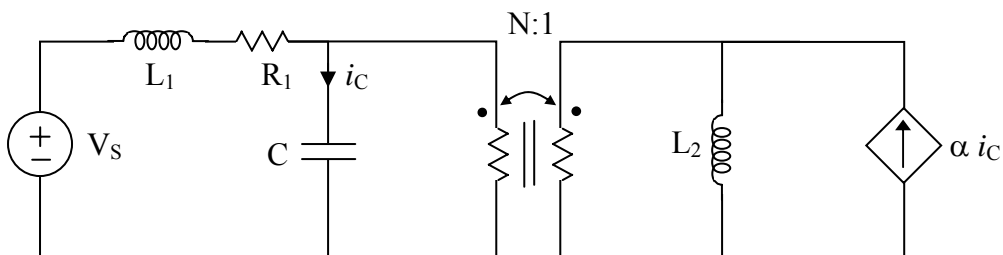4) Obtain the state equations for the circuit.



5)

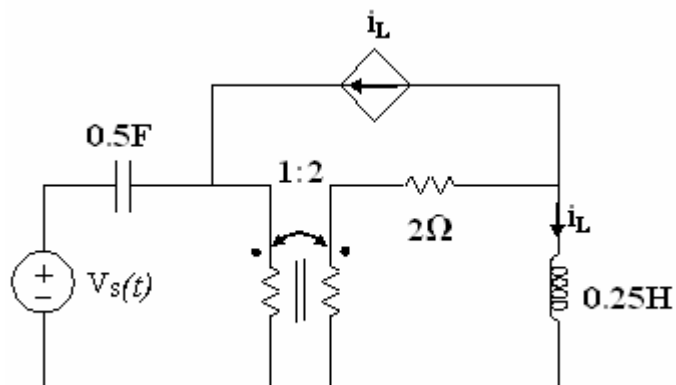

- Find the natural frequencies using MNA.
- Find the natural frequencies using state equations.

**Note :** For part i) you may use symbolic processing capabilities of MATLAB. Type the following to see an example for symbolic evaluation of determinants.

```
>> syms D
matrix M → >> M = [ D+1 5*D ; 2*D D ];
>> det (M)
>> solve (det(M))
```