
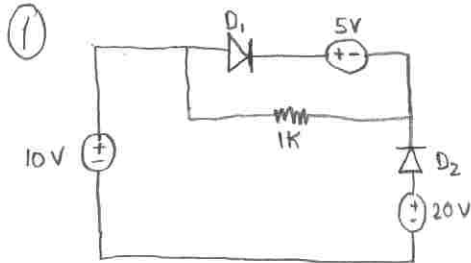


EE 282
HW#1

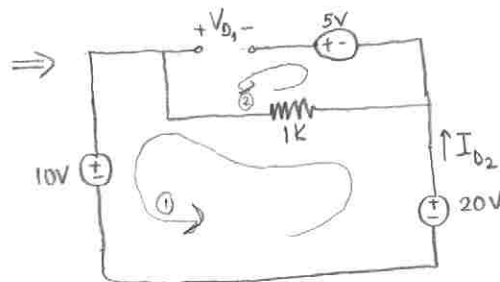

Assume D_1 is OFF and D_2 is ON:




at loop ① by KVL $\rightarrow -20 + 10^3 I_{D2} + 10 = 0$
 $I_{D2} = 10 \text{ mA}$

at loop ② by KVL $\rightarrow -5 - V_{D1} - 10^3 \cdot 10^{-2} = 0$
 $V_{D1} = -15 \text{ V}$


Since $I_{D2} = 10 \text{ mA} > 0$ and $V_{D1} = -15 \text{ V} < 0$, the assumption is true.

Therefore D_1 is OFF and D_2 is ON.

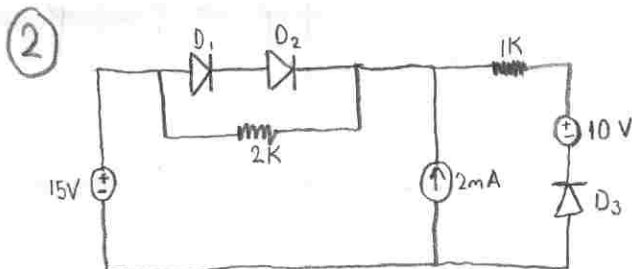

D_1 and D_2 are both on or off. (since if one of them on and the other is off then there will be no current and assumption will be wrong.)

Assume D_1, D_2 and D_3 are all OFF:

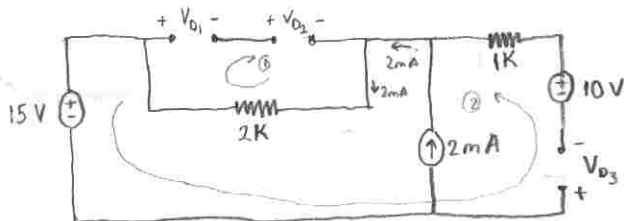

KVL at loop ① $\rightarrow 4 \text{ V} + V_{D1} + V_{D2} = 0$
 $V_{D1} + V_{D2} = -4 \text{ V}$


KVL at loop ② $\rightarrow 15 + V_{D3} - 10 - \underbrace{-V_{D1} - V_{D2}}_{+4 \text{ V}} = 0$
 $15 + V_{D3} - 10 + 4 = 0$
 $V_{D3} = -9 \text{ V}$

Since $V_{D1} < 0, V_{D2} < 0, V_{D3} < 0$, the assumption is true.

Therefore D_1, D_2 and D_3 are all OFF.

II

③

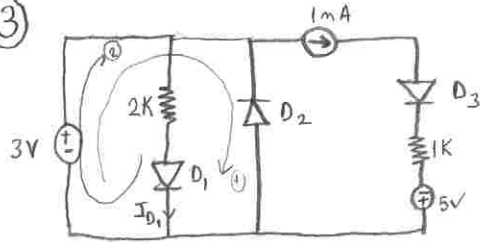

D_3 is on because of the current source.

Assume D_1 and D_3 are ON, D_2 is OFF:









KVL at loop ① : $-3 - V_{D_2} = 0$
 $V_{D_2} = -3V$

KVL at loop ② : $-3 + 2 \cdot 10^3 I_{D_1} + 1 = 0$
 $I_{D_1} = 1mA$


$I_{D_3} = 1mA$






Since $V_{D_2} = -3V < 1V$, $I_{D_1} > 1mA$, $I_{D_3} > 1mA$, the assumption is true.
 Therefore D_1 and D_3 are ON, D_2 is OFF.

④

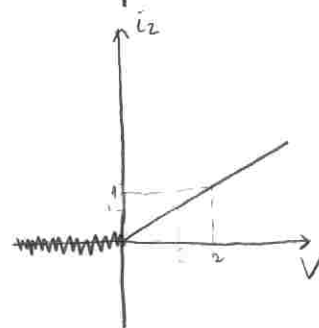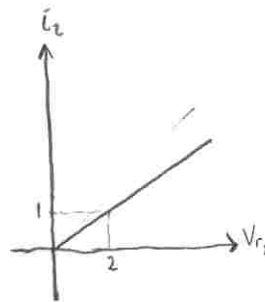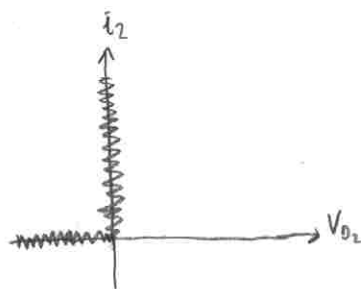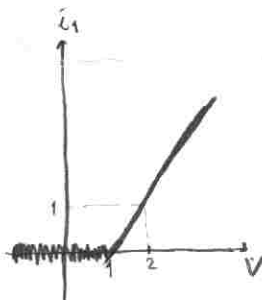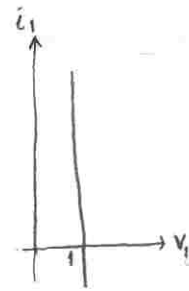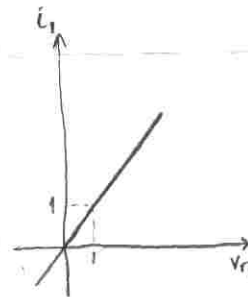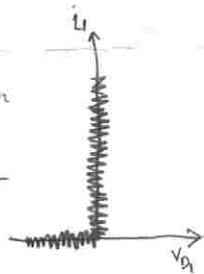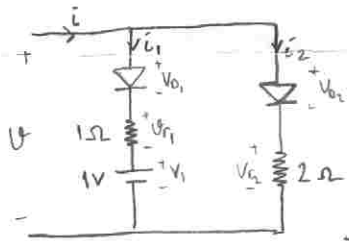

So the i - V characteristic is

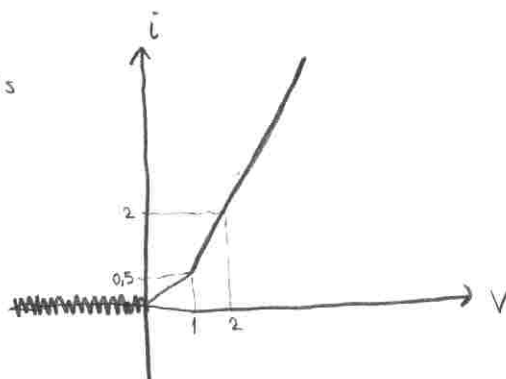

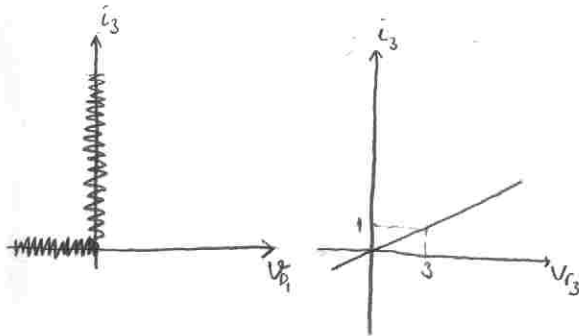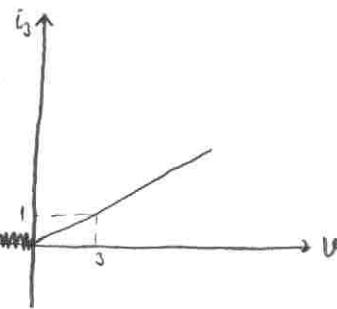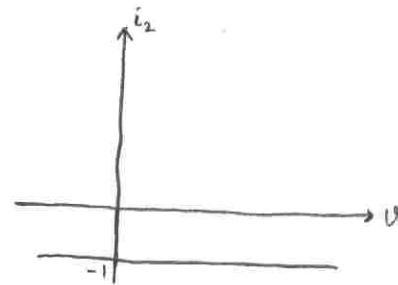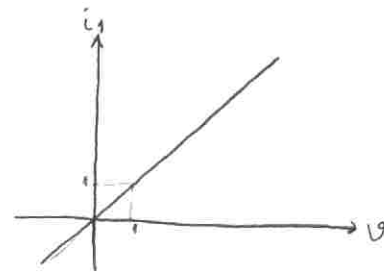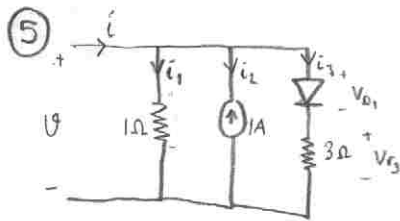

So the i - V characteristic is

