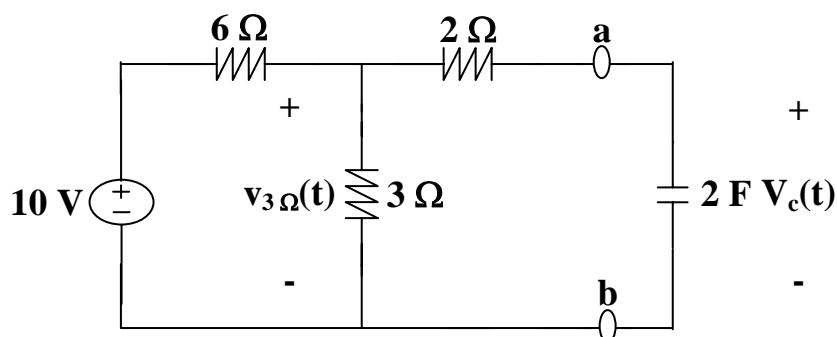



## EE 209 Midterm #2

### Problem 1: (25 pts)



- Find Thevenin Equivalent of the resistive circuit on the left side of a-b terminals.
- Using the result of part a), write a differential equation in terms of  $V_c(t)$  characterizing the given circuit.
- Given that  $V_c(t)$  at  $t=0$  is 2 V, i.e.  $V_c(0)=2$  V; *find and plot*  $V_c(t)$  for  $t \geq 0$ .
- Given that  $V_c(0)=2$  V; *find and plot*  $V_{3\Omega}(t)$  for  $t \geq 0$  using the result of part c).


### Problem 2: (25 pts)

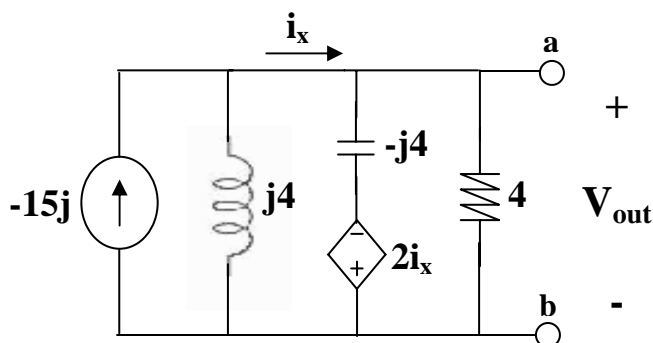

The phasor equivalent of an AC circuit is given above.

- Draw the circuit diagram for the time domain equivalent of the circuit if  $\omega = 2$  rad/sec.
- Find the phasor voltage of  $V_{out}$ .
- Find the steady state value of  $V_{out}(t)$  (take  $\omega = 2$ ).
- Find the equivalent impedance seen from a-b terminals.


**Problem 3: (25pts)**

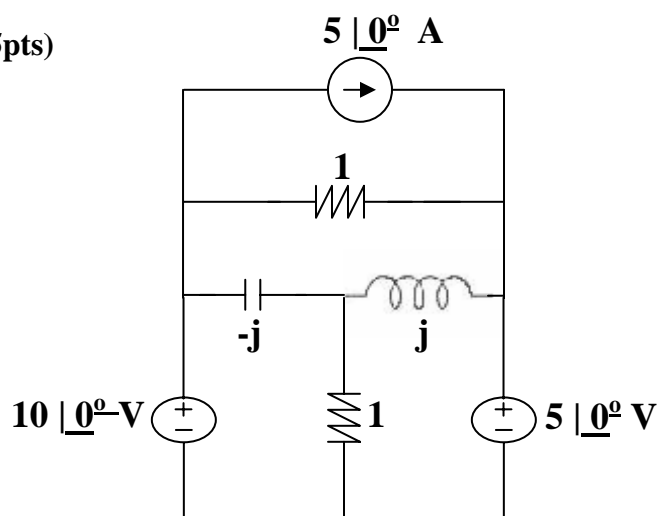

(Voltage and current values are in RMS)

- Find the complex power of each one of the 7 components in the circuit.
- Determine the real power of each source. State whether the source is supplying or absorbing power.
- Determine the power factor of each source. State whether it is lagging or leading.

**Problem 4: (25 pts)**

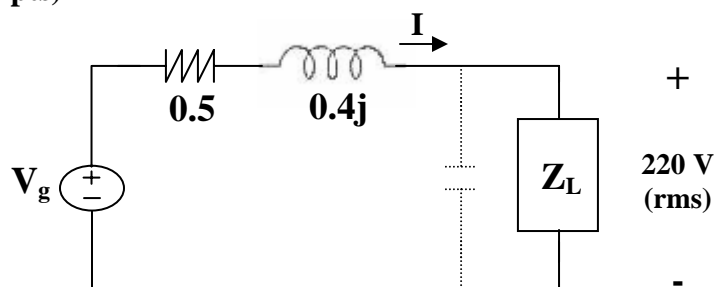

The load shown by  $Z_L$  absorbs 60 kW at 0.8 pf lagging.

For the circuit shown above, a shunt capacitor is being planned to be installed in parallel with the load. (Assume that the load voltage stays at 220 V (rms) after the capacitor installation)

- Find the magnitude of current  $I$ , the power loss on  $0.5\ \Omega$  resistor and the magnitude of voltage  $V_g$ , when there is no shunt capacitor in the system.
- Assume that the connected capacitor improves the power factor of the combined load (the capacitor and  $Z_L$ ) to 0.95 lagging. Redo part a) when the capacitor is in-line.