
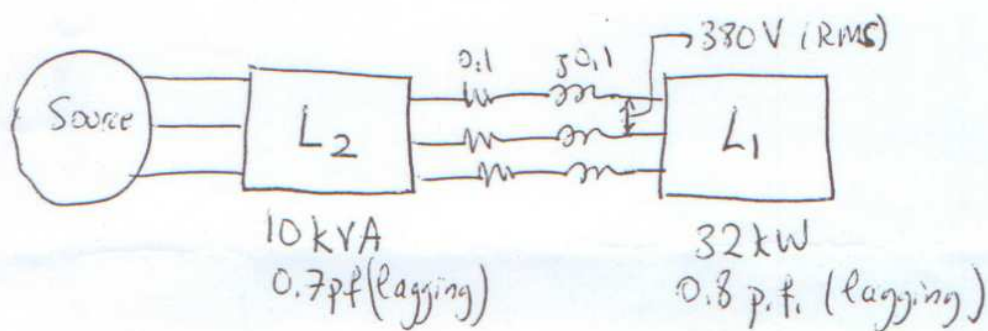


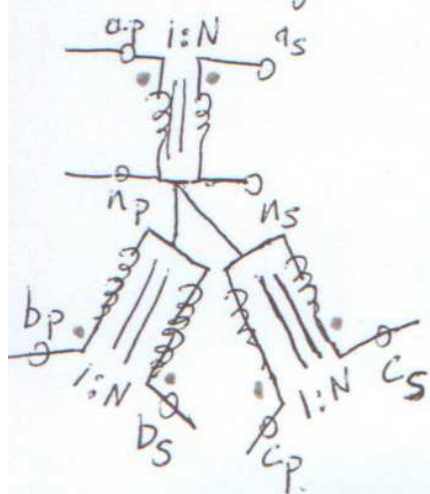- ① A balanced  $3\phi$  load of  $L_1$  of 32 kW at 0.8 p.f. lagging. A second  $3\phi$  load is connected to  $L_1$  through transmission line of impedance  $0.1 + j0.1$ ; The second load  $L_2$  draws 10 kVA at 0.7 p.f. lagging. The voltage across  $L_1$  is given as 380 Volts (RMS) line to line.



- Find line to line voltage across  $L_2$ .
- Find p.f. of the source.

- 2) A  $3\phi$  transformer is a magnetically coupled circuit modifying current/voltage levels on 3 phases.




$a_p$ : line a primary side  
 $a_s$ : line a secondary side

$b_p, b_s$   
 $c_p, c_s$  } similar

$$\frac{V_{a_s n_s}}{V_{a_p n_p}} = \frac{V_{b_s n_s}}{V_{b_p n_p}} = \frac{V_{c_s n_s}}{V_{c_p n_p}} = N$$

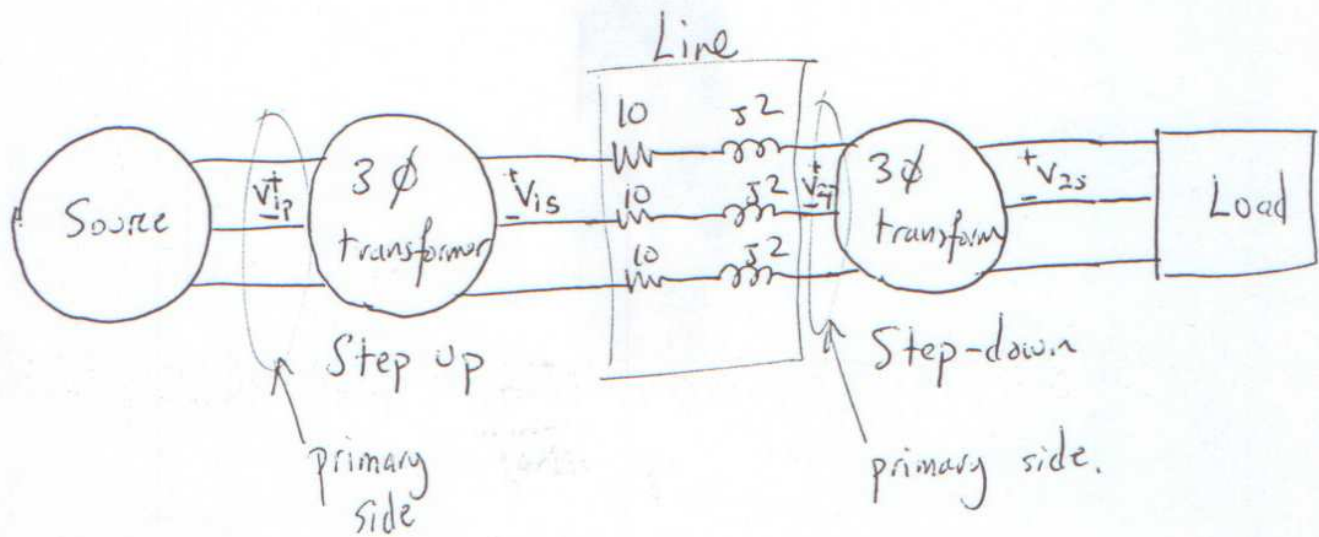Similar for the current (as single phase)



Step-up transformer has higher voltage on secondary side.

Step-down transformer has lower voltage on secondary side,

that is  $\frac{V_{1s}}{V_{1p}} = N$  and  $\frac{V_{2s}}{V_{2p}} = \frac{1}{N}$


If load is  $\Delta$  connected with impedance  $40 + j8 \Omega$  per phase. Source supplies 140 V (RMS) line-to-line.

a) Draw single phase equivalent of the circuit.

b) Find ratio of  $\frac{\text{Power lost on line}}{\text{Power delivered to load}}$  when  $N=1$

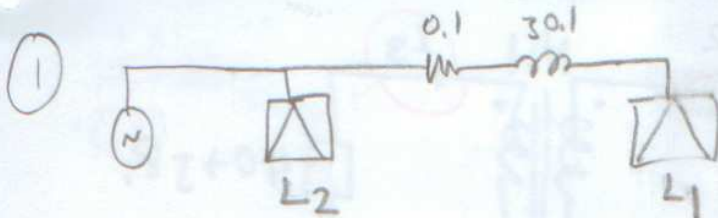c) Find the ratio in part b ; when  $N=10$ .



Simon  
2006/07

$$a) \begin{cases} S_{L1} = 32,000 + j 32,000 \tan(\cos^{-1} 0.8) = 32,000 + j 24,000 \\ S_{L2} = 10,000 \angle 45^\circ = 7070 + j 7070 \end{cases}$$

$$\frac{5}{4} \angle \frac{3}{4}$$

$$\begin{cases} |S_{L1}| = \sqrt{3} |V_{Line}| |I_{Line}| \\ 40,000 = \sqrt{3} |380| |I_{Line}| \rightarrow |I_{Line}| = 60.77 \text{ A} \end{cases}$$

$$\begin{cases} S_{Line} = 3 |I_{Line}|^2 (0.1 + j 0.1) = 1108 + j 1108 \end{cases}$$

$$S_{L1} + S_{Line} = 33108 + j 25108$$


$$|S_{Line \text{ and } L1}| = \sqrt{(33108)^2 + (25108)^2} = \sqrt{3} |V_{Line}| 60.77$$

$$|V_{Line}|^2 = 394.8 \text{ V (rms)}$$

$$b) S_{L1 \text{ and } L2 \text{ and } Line} = (33108 + j 25108) + (7070 + j 7070) = 40178 + j 32178$$

$$p.f. = \cos\left(\tan^{-1} \left| \frac{32178}{40178} \right| \right) = 0.78 \text{ (lagging)}$$

(2)

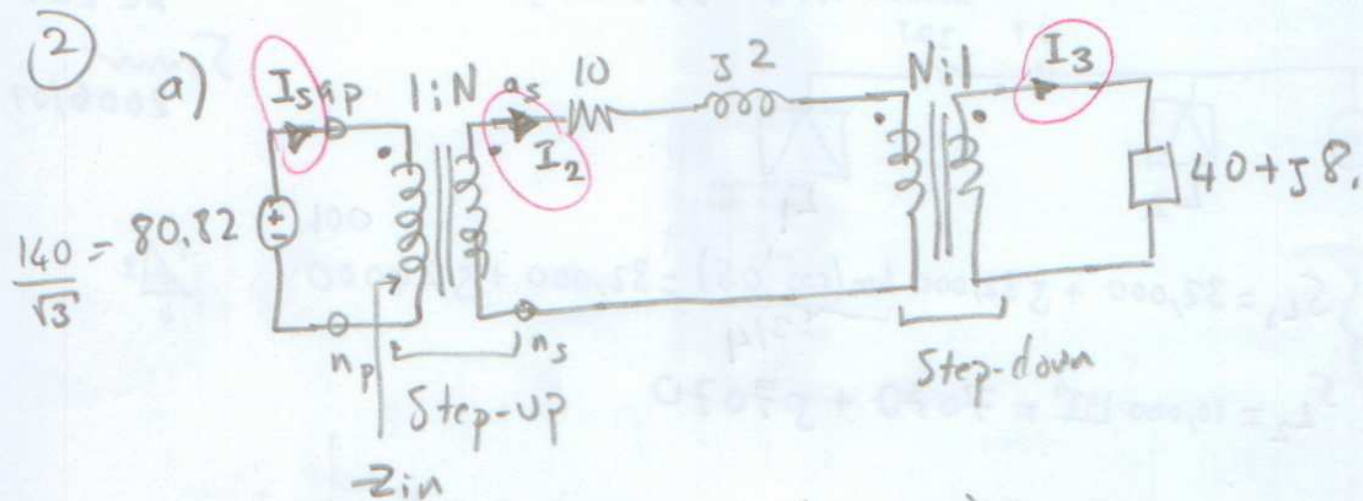

$$b) Z_{in} = (40 + j8) N^2 \cdot \frac{1}{N^2} + (10 + j2) \frac{1}{N^2}$$

$$I_s = \frac{80 \angle 0}{(40 + j8) + (10 + j2) \frac{1}{N^2}} = \frac{80}{(10 + j2) \left( \frac{1}{N^2} + 4 \right)}$$

$$I_2 = I_s \cdot \frac{1}{N} = \frac{80/N}{(10 + j2) \left( \frac{1}{N^2} + 4 \right)}$$

$$I_3 = I_2 \cdot N = I_s$$

$$P_{Line, \text{ per phase }} = |I_2|^2 \cdot 10 = \frac{6400/N^2}{(104) \left( \frac{1}{N^2} + 4 \right)^2} \cdot 10$$

$$P_{Load, \text{ per phase }} = |I_3|^2 \cdot 40 = \frac{6400}{(104) \left( \frac{1}{N^2} + 4 \right)^2} \cdot 40$$

$$b) N=1 \rightarrow \frac{P_{Line}}{P_{Load}} = \frac{1}{4}$$

$$c) N=10; \frac{P_{Line}}{P_{Load}} = \frac{1}{400}$$

So Power lost on line becomes an insignificant ratio of power delivered when  $N=10$ .