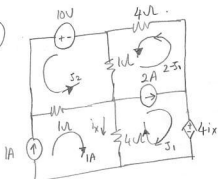


(2)



$$s_2 = i_s$$

Mesh s_2 : $-10 + 1(s_2 + 1) + 1(s_2 + s_1 - 2) = 0$ (1)

Mesh s_1 union Mesh $(2-s_1)$: $4(2-s_1) + 1(2-s_1-s_2) + 4(1-s_1) - 4i_x = 0$ (2)
(Supermesh)

$$i_x = (1 - s_1)$$

(1) : $s_1 + 2s_2 = 11$


(2) : $-5s_1 - s_2 = -10$

$$s_2 = \frac{55-10}{10-1} = \frac{45}{9} = 5A,$$

$I_s = 5A$

Problem 3:

a) V_{oc} :

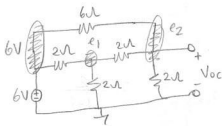

$$e_2 = V_{oc},$$


KCL at e_1 : $\frac{e_1 - 6}{2} + \frac{e_1}{2} + \frac{e_1 - e_2}{2} = 0 \rightarrow 3e_1 - e_2 = 6$

KCL at e_2 : $\frac{e_2}{2} + \frac{e_2 - e_1}{2} + \frac{e_2 - 6}{6} = 0 \rightarrow -3e_1 + 7e_2 = 6$

$$6e_2 = 12$$

$$V_{oc} = e_2 = 2V$$

I_{sc} :

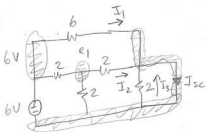


KCL at e_1 : $\frac{e_1 - 6}{2} + \frac{e_1}{2} + \frac{e_1}{2} = 0 \rightarrow e_1 = 2V$

$$I_{sc} = I_1 + I_2 + I_3 = \frac{6-0}{6} + \frac{e_1-0}{2} + \frac{0-0}{2} = 1 + \frac{e_1}{2} = 2A$$

$$R_{Th} = \frac{V_{oc}}{I_{sc}} = \frac{2}{2} = 1\Omega$$


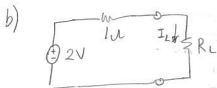
a) $R_L = R_{Th} = 1\Omega$ for maximum power transfer



$$I_L = \frac{2}{1+R_L}$$

$$I_L \text{ for max. power transfer} \Rightarrow \hat{I}_L = \frac{2}{2} = 1A$$

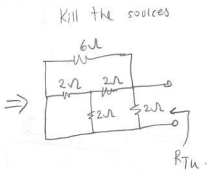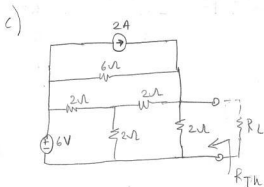
$$\text{Maximum Power} \Rightarrow P_{max} = (\hat{I}_L)^2 \cdot 1 = 1 \text{ Watt.}$$



Note that the circuit in part (a) and in part (c) have the same R_{Th} . Therefore for maximum power transfer $R_L = 1\Omega$ as in part (a).

Then by superposition:

(3c) cont.

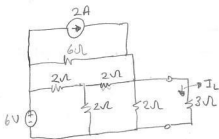


$$I_L = I_{L1} + I_{L2}$$

$$I_L = 1 + 1$$


$$I_L = 2A$$
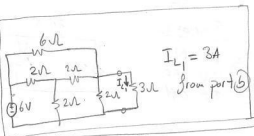
$$P_{max} = (I_L)^2 \cdot 1 = 4 \text{ Watt}$$



$$I_{L1} = 3A$$

from part (b)

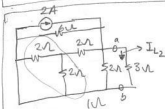

$$I_{L2} = 1A$$



$$I_{L2} = 2 \cdot \frac{1}{\frac{1}{6} + \frac{1}{3} + \frac{1}{2} + 1}$$

$$= 1A$$

$$I_{L2} = 1A$$


Problem 4:

Sources:

4A: ON

10V: OFF

8A: OFF

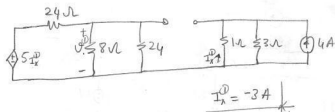


$$v^1 = 5i_1 \cdot \frac{8 \parallel 24}{8 \parallel 24 + 24} = 5(-3) \cdot \frac{6}{6 + 24} = -3V$$

Sources

4A: OFF

10V: ON

8A: OFF

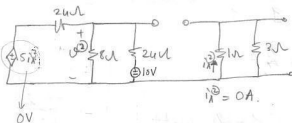


$$v^2 = \frac{10}{24 + 24 \parallel 8} \cdot (24 \parallel 8) = \frac{10}{24 + 6} \cdot 6 = 2V$$

Sources:

4A: OFF

10V: OFF

8A: ON

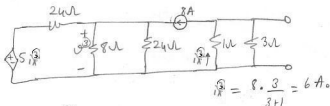

$$v^3 = 5i_1 \cdot \frac{8 \parallel 24}{8 \parallel 24 + 24} + 8 \cdot \left(\frac{24 \parallel 8 \parallel 24}{3+1} \right) = 6 + 8 \cdot \frac{24 \cdot 8 \cdot 24}{3 \cdot 5 \cdot 5} = 44.4$$

$$v = v^1 + v^2 + v^3 = -3 + 2 + 44.4 = 43.4V$$