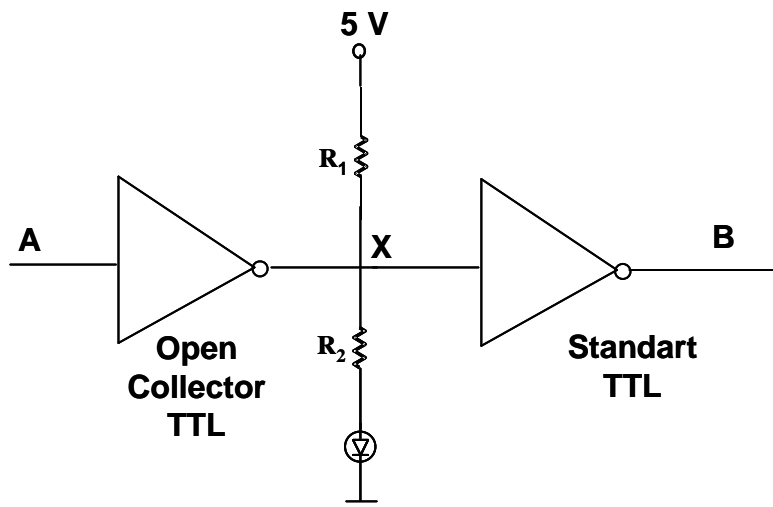




Interfacing Logic Circuits

Q1. A light emitting diode (LED) is a diode which emits light when a forward current flows through it and the brightness of the diode is a function of its forward current. Assume that the LED in the following circuit has a turn on voltage of 0.9 V and requires 1 mA to light.



Open Collector TTL

$$V_{\text{supply}} = 5 \text{ V}$$

$$I_{\text{OH Max}} = 250 \mu\text{A}$$

$$I_{\text{OL Max}} = 20 \text{ mA}$$

$$V_{\text{OL Max}} = 0.4 \text{ V}$$

Standard TTL

$$V_{\text{supply}} = 5 \text{ V}$$

$$I_{\text{IL Max}} = -2 \text{ mA}$$


$$I_{\text{IH Max}} = 250 \mu\text{A}$$

$$V_{\text{IH Min}} = 2.0 \text{ V}$$

$$V_{\text{IL Max}} = 0.8 \text{ V}$$

- Find the minimum value of R_1 so that when the input is high, LED is off and the output B is high.
- Find the maximum value of R_1 so that when the input is low, LED is on (i.e. LED lights) and the output B is low.
- If $R_1 = 1 \text{ k}\Omega$ and $R_2 = 500 \Omega$, how many standard TTL loads can be connected at point X.

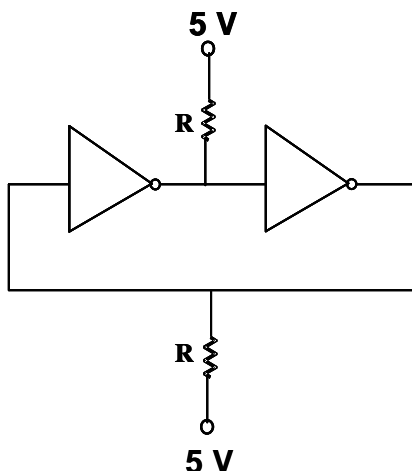Q2. Find an interval for R so that the following circuit, with two open collector TTL inverters, serves as an one bit memory unit.



Open Collector TTL

$$V_{\text{supply}} = 5 \text{ V}$$

$$I_{\text{OH Max}} = 250 \mu\text{A}$$

$$I_{\text{OL Max}} = 20 \text{ mA}$$

$$V_{\text{OL Max}} = 0.4 \text{ V}$$

$$I_{\text{IL Max}} = -2 \text{ mA}$$

$$I_{\text{IH Max}} = 250 \mu\text{A}$$

$$V_{\text{IH Min}} = 2.0 \text{ V}$$

$$V_{\text{IL Max}} = 0.8 \text{ V}$$