
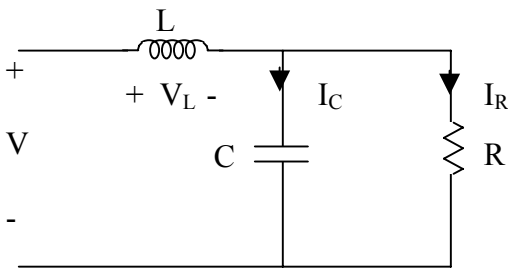
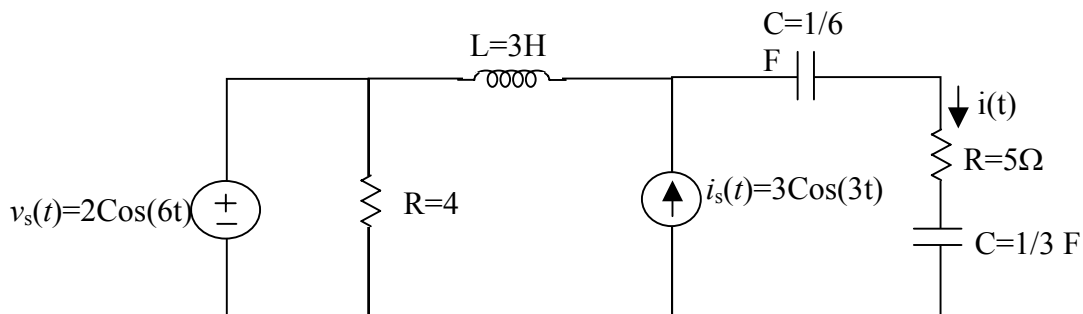


1)

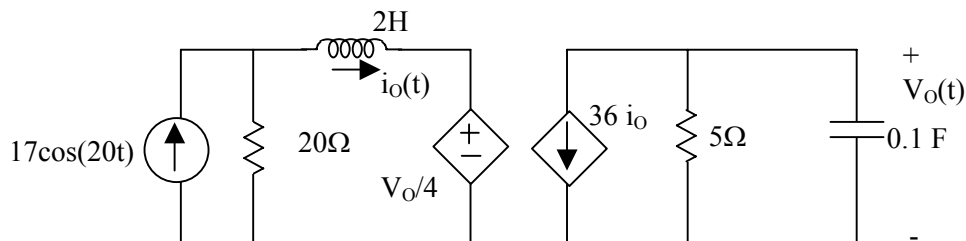

$$R = 100 \, \Omega, \quad Z_L = j200 \, \Omega, \quad Z_C = -j200 \, \Omega, \quad \omega = 6000 \, \text{rad/s}.$$

- Find the input admittance at this frequency.
- Take the angle of I_R as the reference for phase and draw a phasor diagram that includes the voltage and current phasors of each element.
- Find the angular frequencies at which the impedance will be purely real.

2) Find the current $i(t)$ when the circuit is in steady-state.3) Find the steady state values of for $i_o(t)$ and $V_o(t)$ by using node analysis in phasor domain.4) Given the circuit below, find $i_R(t)$ for sinusoidal steady state.