


EE 202: Circuit Theory II

2007-2008 Spring Semester
Midterm I
March 27, 2008

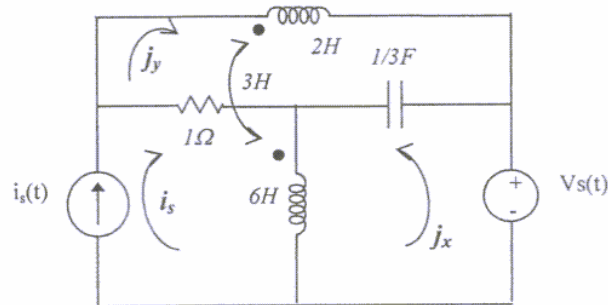Q1) (25pts)

For the following circuit;

- Write the mesh equations (in time domain) using the shown mesh currents. Express equations in the matrix form.
- Find the natural frequencies.
(Assume that all initial conditions are zero.)




Q2) (15pts)

In the circuit given below, Y_1 and Y_2 blocks are a single circuit component either R or L or C. The branch current I_1 is in phase with E and its magnitude, $|I_1|$ is 3 A.


The source voltage E has magnitude, $|E|$, equal to 120 V. The phase of voltage source is unknown, but it is known that E leads the current $I_T = 5e^{j45^\circ}$ A.

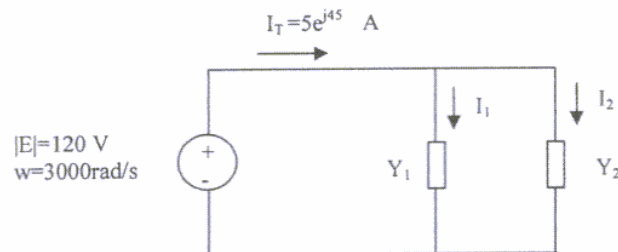Find the value of each element and the equivalent simple series circuit at the given frequency.




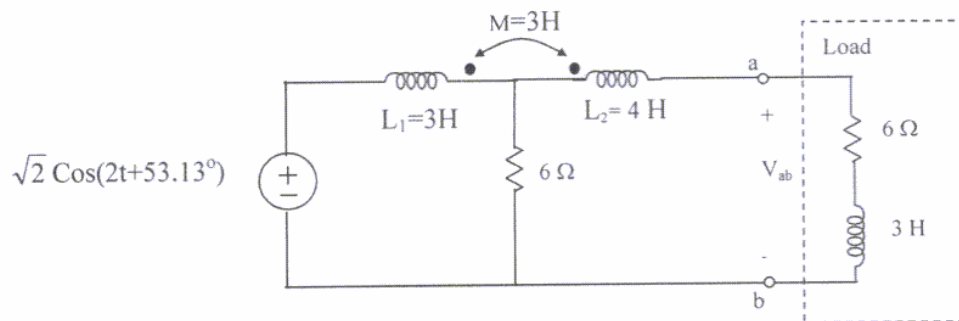Q3) (20pts) For the following circuit,


- Find Thevenin equivalent circuit with respect to the a-b terminals.
- Find the average power delivered to the load the load.




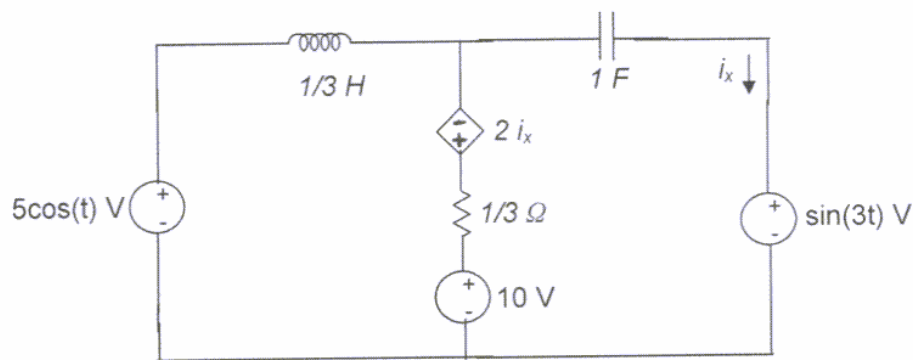Q4) (20pts) Find $i_x(t)$ at steady-state.



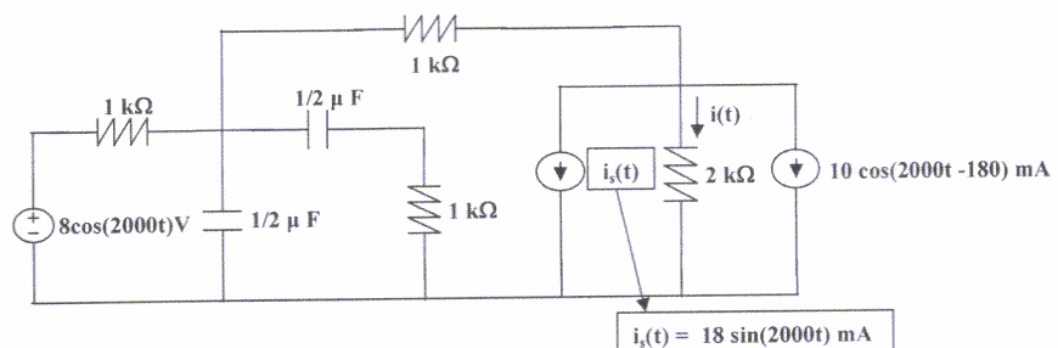Q5) (20 pts) Find $i(t)$ at steady-state.



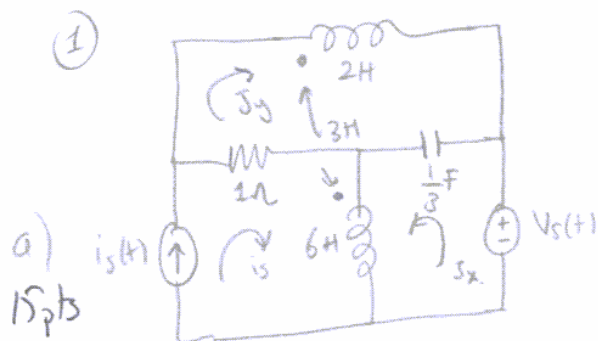

Mesh i_y : $2D i_y + 3D(i_x + i_s) + 3D^{-1}(i_x + i_y) + (i_y - i_s) = 0$

Mesh i_x : $-V_s(t) + 3D^{-1}(i_x + i_y) + 6D(i_x + i_s) + 3D i_y = 0$

$$\begin{bmatrix} 3D + 3D^{-1} & 2D + 1 + 3D^{-1} \\ 3D^{-1} + 6D & 3D^{-1} + 3D \end{bmatrix} \begin{bmatrix} i_x \\ i_y \end{bmatrix} = \begin{bmatrix} i_s(t) - 3D i_s(t) \\ V_s(t) - 6D i_s(t) \end{bmatrix}$$

b) Assume ω pts.

$$\begin{bmatrix} i_x \\ i_y \end{bmatrix} = \begin{bmatrix} A \\ B \end{bmatrix} e^{\lambda t} \rightarrow \underbrace{\begin{bmatrix} 3\lambda + \frac{3}{\lambda} & 2\lambda + 1 + \frac{3}{\lambda} \\ \frac{3}{\lambda} + 6\lambda & \frac{3}{\lambda} + 3\lambda \end{bmatrix}}_A \begin{bmatrix} A \\ B \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \end{bmatrix}$$

$$|A| = \left| \begin{bmatrix} 3\lambda + \frac{3}{\lambda} & 2\lambda + 1 + \frac{3}{\lambda} \\ 3\lambda & \lambda - 1 \end{bmatrix} \right| = \left| \begin{bmatrix} \lambda - 1 & 2\lambda + 1 + \frac{3}{\lambda} \\ 2\lambda + 1 & \lambda - 1 \end{bmatrix} \right|$$

$$= (\lambda - 1)^2 - \frac{(2\lambda + 1)^2 - 3(2\lambda + 1)}{\lambda}$$


$$= 3\lambda(-\lambda - 2) - \frac{6\lambda + 3}{\lambda}$$

$$= -3\lambda^3 - 6\lambda^2 - 6\lambda - 3$$

$$\begin{aligned} &\rightarrow |A| = 0 \\ &\downarrow \\ &\lambda^3 + 2\lambda^2 + 2\lambda + 1 = 0 \\ &(\lambda + 1)(\lambda^2 + \lambda + 1) = 0 \\ &\lambda = \left\{ -1, \frac{-1 \pm \sqrt{3}j}{2} \right\} \end{aligned}$$

Problem 2 :

2

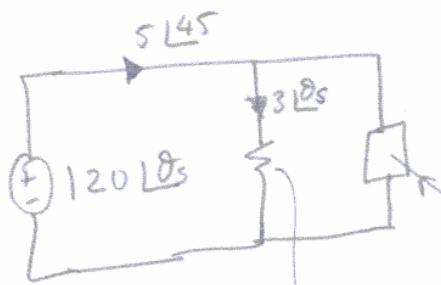

Y_2 : Inductor - since E leads the current.
($\theta_s > 45^\circ$).

R : since current is in phase with source

$$R = 40 \Omega$$

$$|I_T| = \frac{120}{|Z_{tot}|} = 5 \rightarrow |Z_{tot}| = 24 \rightarrow |Y_{tot}| = \frac{1}{24}$$

$$R \parallel j\omega L$$


40Ω 3000

$$Y_{tot} = \frac{1}{40} + \frac{-j}{\omega L}$$

$$|Y_{tot}| = \sqrt{\left(\frac{1}{40}\right)^2 + \left(\frac{1}{\omega L}\right)^2} = \frac{1}{24}$$

$$\left(\frac{1}{\omega L}\right)^2 = \left(\frac{1}{24}\right)^2 - \left(\frac{1}{40}\right)^2 = \left(\frac{1}{8}\right)^2 \left(\frac{1}{9} - \frac{1}{25}\right) = \frac{16}{64 \cdot 9 \cdot 25}$$
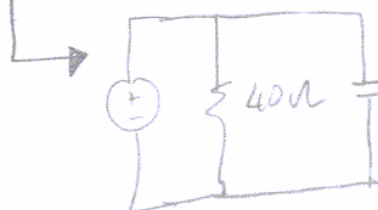
$$\omega L = 30 \leftarrow \frac{1}{\omega L} = \frac{4}{8 \cdot 3.5}$$




$$L = \frac{30}{3000} = 10 \text{ mH}$$

$$40 \parallel -j30 = 10(4 \parallel -j3) = 10 \cdot \frac{4 \cdot (-j3)}{4 - j3} = 24 \angle 32^\circ$$

Problem 3:


3

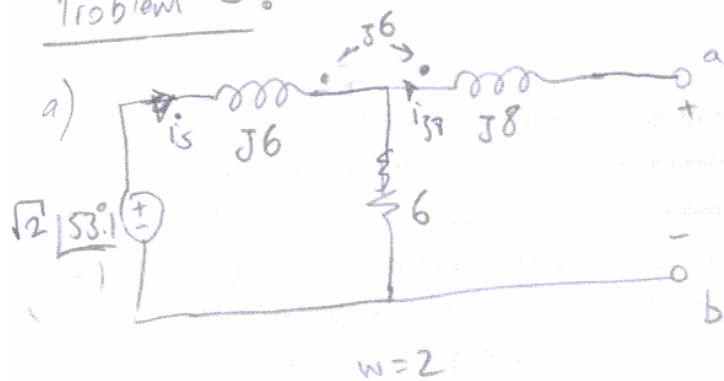

$$V_{oc} : ? \quad i_{s8} = 0 \rightarrow i_s = \frac{\sqrt{2} \angle 53.1^\circ}{j6 + 6} = \frac{\sqrt{2} \angle 53.1^\circ}{6\sqrt{2} \angle 45^\circ} = \frac{1}{6} \angle 8.1^\circ$$

$$V_{oc} = \overbrace{6 i_s}^{V_{6\Omega}} - \overbrace{(-j6 i_s)}^{V_{j8}} = (6 + j6) i_s = \sqrt{2} \angle 53.1^\circ$$

$i_{sc} : ?$

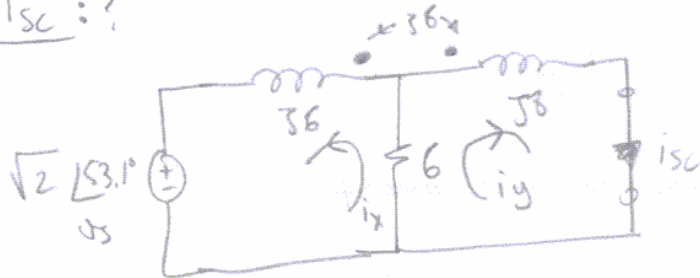

$$\text{Mesh } i_x : 6(i_x + i_y) + j6 i_x + j6(i_y) = -V_s \quad (1)$$

$$\text{Mesh } i_y : 6(i_x + i_y) + j8 i_y + j6(i_x) = 0 \quad (2)$$

$$(1) - (2) \rightarrow -j2 i_y = -V_s \rightarrow i_y = \frac{\sqrt{2} \angle 53.1^\circ}{-j2}$$


$$i_{sc} = i_y \leftarrow i_y = \frac{1}{\sqrt{2}} \angle -37^\circ$$

$$Z_{Th} = \frac{\sqrt{2} \angle 53.1^\circ}{\frac{1}{\sqrt{2}} \angle -37^\circ} = j2 \Omega$$

Problem 3;

4


Part b)

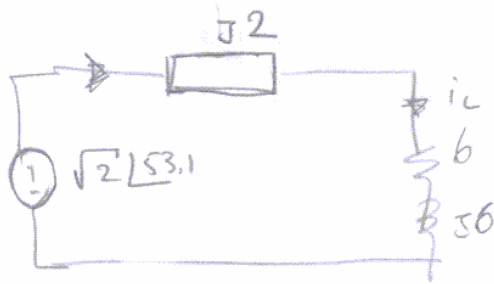

$$i_L = \frac{\sqrt{2} \angle 53.1^\circ}{6 + j8} = \frac{\sqrt{2} \angle 53.1^\circ}{10 \angle 53.1^\circ} = \frac{\sqrt{2}}{10}$$

$$P_{\text{Load delivered}} = \frac{1}{2} |i_L|^2 \cdot 6 = \frac{6}{100} \text{ Watts.}$$

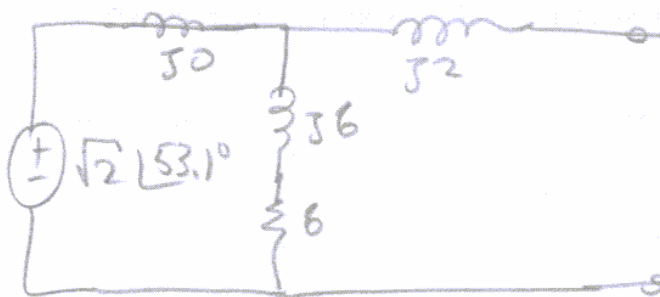Easier way: Insert T-model for mutual inductor.




$$\left. \begin{array}{l} V_{oc} = \sqrt{2} \angle 53.1^\circ \\ R_{Th} = j2 \end{array} \right\} \text{ by inspection.}$$

Problem 4:


5

- ① DC: ON
 $u=1$: OFF
 $u=3$: OFF

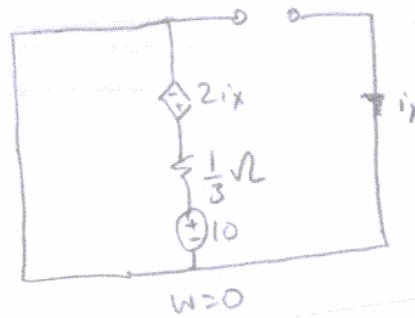

$i_x^{(1)} = 0$

- ② DC: OFF
 $u=1$: ON
 $u=3$: OFF

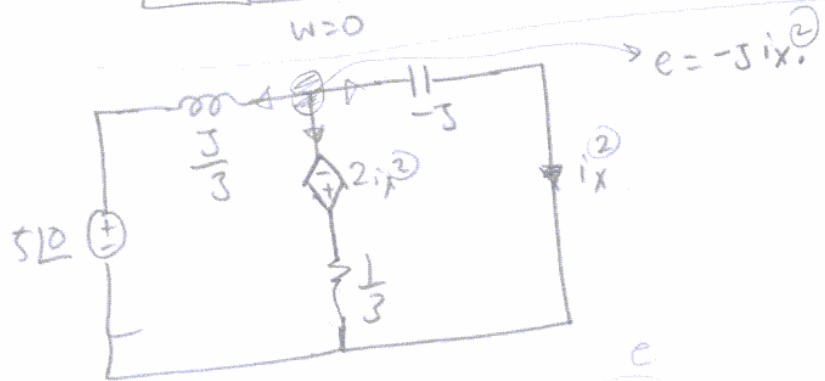

$$\frac{-j i_x^{(2)} + 2 i_x^{(2)}}{1/3} + i_x^{(2)} + \frac{-j i_x^{(2)} - 5}{j/3} = 0$$

$$i_x^{(2)} \left(-j + 2 + \frac{1}{3} + 1 \right) = -5j$$


$$i_x^{(2)} \left(\frac{4 - 3j}{3} \right) = -5j$$

$$i_x^{(2)} = -3j \angle \tan^{-1} 3/4 \rightarrow 37^\circ$$

$$i_x^{(2)} = 3 \angle 90 + 37^\circ = 3 \angle 53^\circ$$

$$i_x^{(2)}(t) = 3 \cos(t - 53^\circ) \text{ V}$$

- ③ DC: OFF
 $u=1$: OFF
 $u=3$: ON

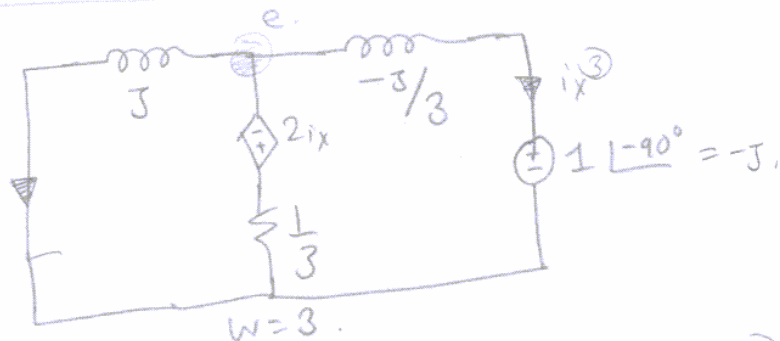

$$\frac{e}{j} + \frac{e + 2 i_x^{(3)}}{1/3} + \frac{e - (-j)}{-j/3} = 0 \rightarrow e(-j + 3 + 3j) = +3 - 6 i_x^{(3)}$$

(6)

$$\left(-j - \frac{j}{3} i_x^{(3)}\right)(2j + 3) = 3 - 6 i_x^{(3)}$$

$$-j(3 + i_x)(2j + 3) = 9 - 18 i_x^{(3)}$$

$$i_x^{(3)}(20 - 3j) = 3 + 9j$$

$$i_x^{(3)} = \frac{3 + 9j}{20 - 3j} = \frac{3\sqrt{10} \angle \tan^{-1} 3}{\sqrt{409} \angle -\tan^{-1} 3/20}$$

$$i_x^{(3)} = 3\sqrt{\frac{10}{409}} \cos\left(3t + \tan^{-1} 3 + \tan^{-1} \frac{3}{20}\right) \text{ V.}$$

$$i_f(t) = i_x^{(1)}(t) + i_x^{(2)}(t) + i_x^{(3)}(t)$$

$$= 3 \cos(t + 53^\circ) + 3\sqrt{\frac{10}{409}} \cos\left(3t + \tan^{-1} 3 + \tan^{-1} \frac{3}{20}\right) \text{ V.}$$

