


EE202 Homework 2 (Due Tuesday, March 18, 2008)

**Solve problems 9.11, 9.23, 9.38, 9.41, 9.44, 9.57, 9.69 (given below)
from Nilsson and Riedel, 7th edition.**

- 9.23 a) Show that, at a given frequency ω , the circuits in Fig. P9.23(a) and (b) will have the same impedance between the terminals a,b if

$$R_1 = \frac{\omega^2 L_2^2 R_2}{R_2^2 + \omega^2 L_2^2}, \quad L_1 = \frac{R_2^2 L_2}{R_2^2 + \omega^2 L_2^2}$$


Figure P9.23

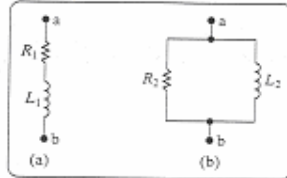

- b) Find the values of resistance and inductance that when connected in series will have the same impedance at 4 krad/s as that of a 5 k Ω resistor connected in parallel with a 1.25 H inductor.

- 9.38 Find I_b and Z in the circuit shown in Fig. P9.38 if $V_g = 25 \angle 0^\circ$ V and $I_b = 5 \angle 90^\circ$ A.


Figure P9.38

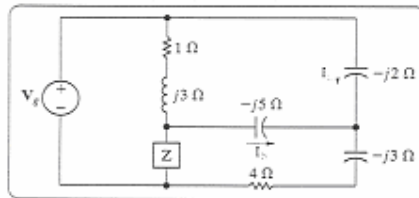

- 9.41 The sinusoidal voltage source in the circuit in Fig. P9.41 is developing a voltage equal to $247.49 \cos(1000t + 45^\circ)$ V.


- Find the Thévenin voltage with respect to the terminals a,b.
- Find the Thévenin impedance with respect to the terminals a,b.
- Draw the Thévenin equivalent.

Figure P9.41

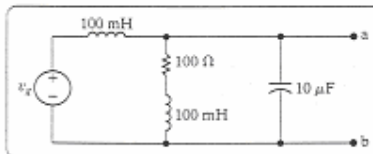

- 9.44 Find the Norton equivalent with respect to terminals a,b in the circuit of Fig. P9.44.


Figure P9.44

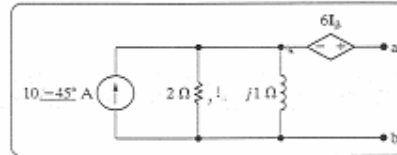

9.57


Use the node-voltage method to find V_o and I_o in the circuit seen in Fig. P9.57.

Figure P9.57

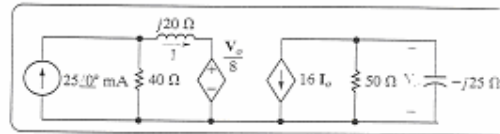

- 9.69 The value of k in the circuit in Fig. P9.69 is adjusted so that Z_{ab} is purely resistive when $\omega = 4$ krad/s. Find Z_{ab} .

Figure P9.69

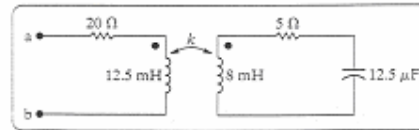

- 11 Use the concept of the phasor to combine the following sinusoidal functions into a single trigonometric expression:

- $y = 50 \cos(300t + 60^\circ) + 100 \cos(500t - 30^\circ)$.
- $y = 200 \cos(377t + 50^\circ) - 100 \sin(377t + 150^\circ)$.
- $y = 80 \cos(100t + 30^\circ) - 100 \sin(100t - 135^\circ) + 50 \cos(100t - 90^\circ)$, and
- $y = 250 \cos \omega t + 250 \cos(\omega t + 120^\circ) + 250 \cos(\omega t - 120^\circ)$.